

HOCHSCHULE RHEINMAIN



PHYSICS LAB 3

---

# Experiment P3-2

## Signal Propagation in Coaxial Cables

---

Authors

CIHAN ÜNLÜ

DENNIS HUNTER

SEBASTIAN KRESS

DEPARTMENT OF ENGINEERING

APPLIED PHYSICS & MEDICAL TECHNOLOGY

Date of experiment:   Dezember 1st, 2020  
Date of submission:   December 16, 2020

# Contents

<b>1</b>	<b>Introduction</b>	<b>3</b>
1.1	Terms and Definitions . . . . .	3
1.2	Preparation . . . . .	4
<b>2</b>	<b>Set-Up of Experiment</b>	<b>6</b>
<b>3</b>	<b>Execution</b>	<b>7</b>
<b>4</b>	<b>Evaluation</b>	<b>8</b>
<b>5</b>	<b>Conclusion</b>	<b>9</b>
	<b>List of Figures</b>	<b>10</b>
	<b>List of Tables</b>	<b>11</b>
	<b>List of Symbols</b>	<b>12</b>
<b>A</b>	<b>Appendix</b>	<b>13</b>
	<b>Bibliography</b>	<b>15</b>

# 1 Introduction

## 1.1 Terms and Definitions

### Transmission Line

In their simplest form cables are made out of a conducting material to transport electrical energy or signals from point A to point B. The higher the frequency of the signal to transmit, the less the wave nature of can be neglected.

### Characteristic Impedance, Velocity Factor and Propagation Speed

Characteristic impedance: The impedance, when connected to a transmission line, suppresses any reflections and standing waves [1]. Velocity factor: Relative signal propagation speed inside a transmission line expressed as percent of speed of light. Propagation speed: The absolute speed at which a signal propagates through a medium.

### Time Domain Reflectometry

A method to inspect properties of a transmission line i.e. length, characteristic impedance and velocity factor as well as the presence, nature and location of defects.

### Avalanche Pulse Generator

A circuit to generate ultra short pulses on a scale of picoseconds. Its main working principle abuses the avalanche breakdown of a transistor across the collector-emitter line. The breakdown voltage is usually much higher than the voltages during normal operation.

### Boost Converter

A circuit capable of *boosting* a constant current input voltage to a much higher output voltage by repeatedly switching an inductor on and off. The fly back voltage induced by the break down of the magnetic field gets stored in a capacitance and forms the voltage at the output terminals.

### Pulse Width Modulation

A constant current switched on and off at a fixed frequency. The time the signal is considered high relatively to the period time is called the duty cycle.

### Amplitude, Rise Time, Fall Time, Pulse Width

Text

### Bandwidth and Rise Time of an Oscilloscope

Text

## 1.2 Preparation

### Reflection on a Transmission Line

!!! Insert Diagram Here !!!

### SPICE-Simulation of a Boost Converter

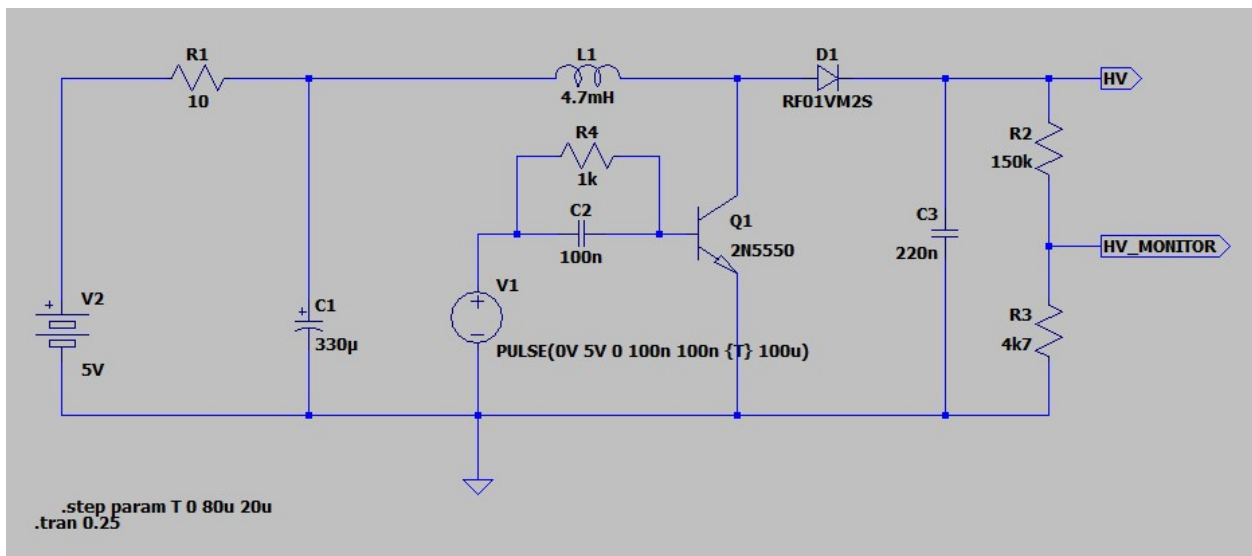


Figure 1.1: Simulated circuit of a boost converter using LTSPICE.

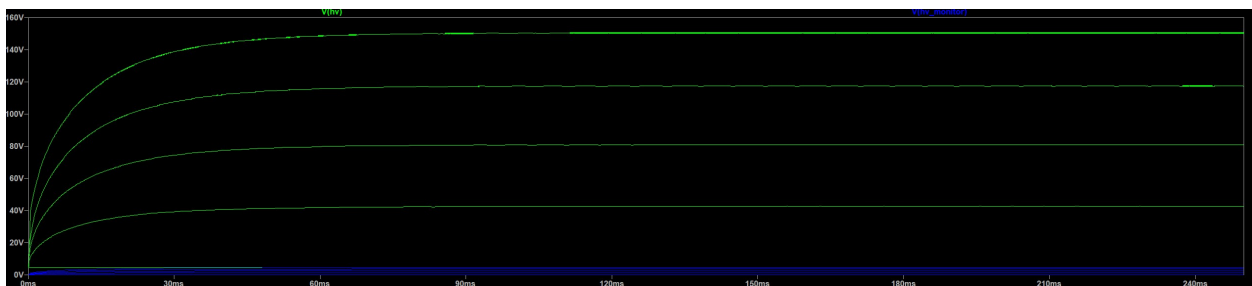


Figure 1.2: Plot of the output voltage at  $HV$ . The voltage is subsequently progressing towards a peak voltage of  $\hat{U}_{HV} \approx 150\text{ V}$  for various PWM duty cycles.

### Charge/Discharge Time of a Capacitor

Charging:

$$\begin{aligned}
 U_{Br} &= U_+ \left( 1 - e^{-\frac{t_{charge}}{R_6 C_5}} \right) \\
 &\Leftrightarrow \\
 t_{charge} &= -\ln \left( 1 - \frac{U_{Br}}{U_+} \right) \cdot R_6 C_5
 \end{aligned} \tag{1.1}$$

Discharging:

$$\begin{aligned}
 U_{C_5} &= U_{Br} \left( e^{-\frac{t_{discharge}}{R_7 C_5}} \right) \\
 &\Leftrightarrow \\
 t_{discharge} &= -\ln \left( \frac{U_{C_5}}{U_{Br}} \right) \cdot R_7 C_5
 \end{aligned} \tag{1.2}$$

plugging in the values for  $U_{Br} = 65 \text{ V}$ ,  $U_+ = 75 \text{ V}$ ,  $U_{C_5} = 5 \text{ V}$ ,  $C_5 = 2.2 \text{ pF}$ ,  $R_6 = 1 \text{ M}\Omega$  and  $R_7 = 51 \Omega$  equates to the following charging/discharging times  $t_{charge}$  and  $t_{discharge}$ :

$$\begin{aligned}
 t_{charge} &= -\ln \left( 1 - \frac{65 \text{ V}}{75 \text{ V}} \right) \cdot 10^6 \Omega \cdot 2.2 \cdot 10^{-12} \text{ F} \\
 &\approx 4.43 \cdot 10^{-6} \text{ s}
 \end{aligned} \tag{1.3}$$

$$\begin{aligned}
 t_{discharge} &= -\ln \left( \frac{5 \text{ V}}{65 \text{ V}} \right) \cdot 51 \Omega \cdot 2.2 \cdot 10^{-12} \text{ F} \\
 &\approx 2.88 \cdot 10^{-10} \text{ s}
 \end{aligned} \tag{1.4}$$

With these numbers, the minimum time per charge/discharge cycle would be the sum of both times. Thus, the maximum number of repetitions per second  $f_{Rep}$  is

$$f_{Rep} = (t_{charge} + t_{discharge})^{-1} \approx 225.7 \text{ kHz} \tag{1.5}$$

## Cable Characteristics of RG-58/U Coaxial Cable

Nominal characteristic impedance:  $53 \Omega$

Nominal velocity of propagation: 69.5%

Nominal delay (translates to the inverse of the absolute speed of propagation):  $4.85588 \text{ ns/m}$

The values above are taken from the technical datasheet [2].

## Determining the Suitability of the Oscilloscope

### Sampling Rate

## **2 Set-Up of Experiment**

## 3 Execution

## 4 Evaluation



## **5 Conclusion**

## List of Figures

1.1	Simulated circuit of a boost converter. . . . .	4
1.2	Plot of the output voltage at $HV$ . The voltage is subsequently progressing towards a peak voltage of $\hat{U}_{HV} \approx 150$ V for various PWM duty cycles. . . . .	4
A.1	Oszillograms . . . . .	13

## List of Tables

A.1	Handwritten notes . . . . .	14
A.1	Handwritten notes . . . . .	14
A.1	Handwritten notes . . . . .	14

# List of Symbols

$A$  Distinct event

# A Appendix

**Figure A.1:** During the course of the experiment captured oscillograms.

**Table A.1:** Handwritten notes corresponding each measurement.

**Table A.1:** Handwritten notes corresponding each measurement.

**Table A.1:** Handwritten notes corresponding each measurement.

## Bibliography

- [1] ATIS. *ATIS Telecom Glossary. American National Standard T1.523-2001*. ATIS.
- [2] Belden. *82240 Coax - RG-58/U Type technical Datasheet*. URL: <https://catalog.belden.com/techdatam/82240.pdf> (visited on 10/12/2020).